

STAIR CASE WIRING

AIM:

To develop and test the staircase wiring using proteus

APPARATUS REQUIRED:

Laptop with proteus software

THEORY:


Staircase wiring is a common multiple way switching or two way switching connection. It involves wiring for one light with two switches. In this set up is controlled by two switches located operates the lead from separate position above or below the staircase from inside or outside of room or two way led switch.

PROCEDURE:

- Drag the required components from the proteus library.
- Connect the components as per circuit diagram.
- Run the simulation and check the lamp for different switching condition.

Staircase Wiring



Circuit Diagram:

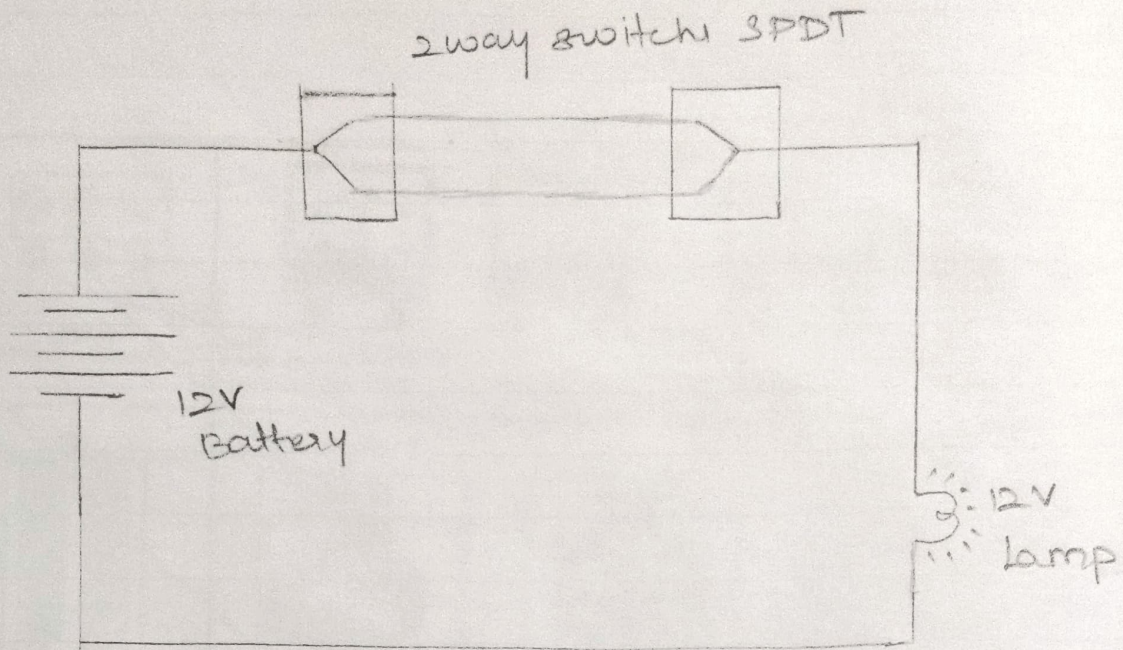

SPDT - Single pole double Throw switch.

Mode	S ₁	S ₂	Lamp
1	ON	ON	ON
2	ON	OFF	OFF
3	OFF	ON	OFF
4	OFF	OFF	ON

Components	Proteus	Specification
AC supply	vsine	Amplitut _{230V}
Two-way switch	SPDT	Frequency 50HZ
Lamp	Animated	230V

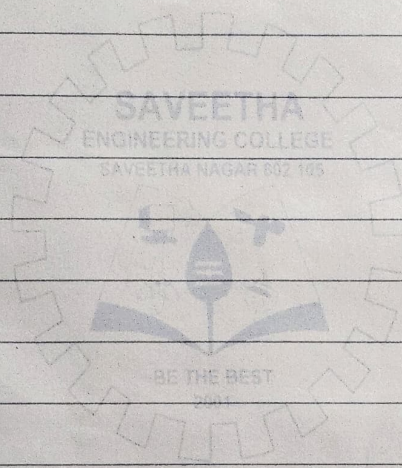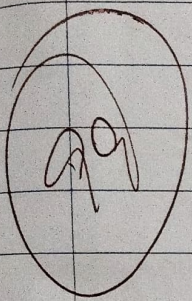


20/10/20

RESULT:

Thus the staircase using connection were developed and tested successfully.

Cross Connection

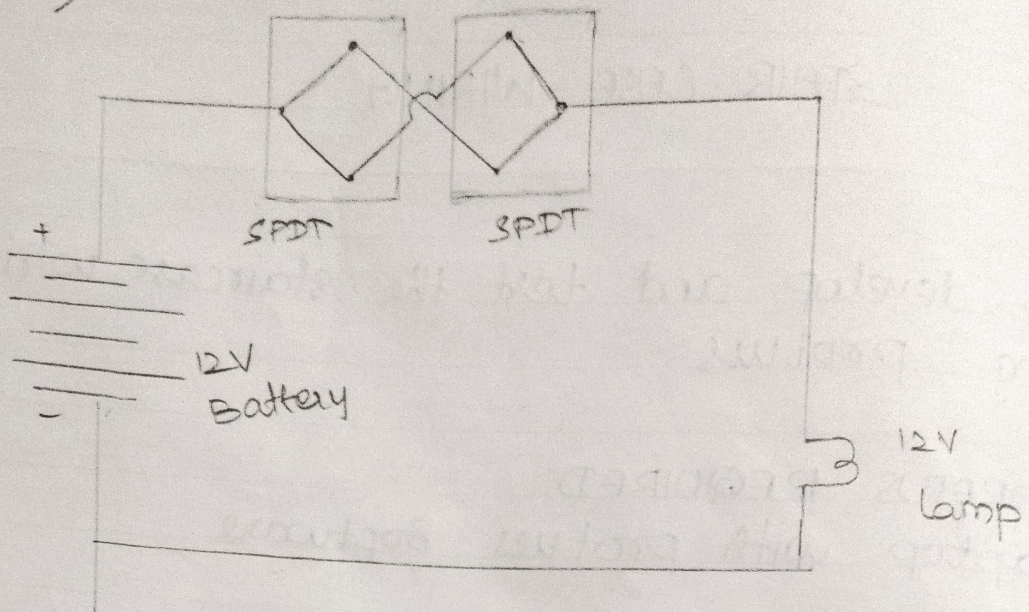

Mode	S_1	S_2	Lamp
1	ON	ON	OFF
2	ON	OFF	ON
3	OFF	ON	ON
4	OFF	OFF	OFF

